

CBCS Scheme

USN

--	--	--	--	--	--	--	--	--	--

15CS32

Third Semester B.E. Degree Examination, June/July 2018 Analog and Digital Electronics

Time: 3 hrs.

Max. Marks: 80

Note: Answer any FIVE full questions, choosing one full question from each module.

Module-1

- 1 a. What is MOSFET? Name its types. Explain the construction of n-channel E-MOSFET. (06 Marks)
b. Compare JFET and MOSFET. (05 Marks)
c. Explain self-bias circuit for JFET. (05 Marks)

OR

- 2 a. Define: i) CMRR ii) Slew rate iii) PSRR iv) Bandwidth pertaining to OPAMP. (06 Marks)
b. Explain with schematics operation of relaxation oscillator with relevant waveforms. (05 Marks)
c. What are active filters? Explain active low pass filter. (05 Marks)

Module-2

- 3 a. Using Q-M method, simplify the expression $f(A, B, C, D) = \sum(0, 3, 5, 6, 7, 11, 14)$. (06 Marks)
b. Explain about positive and negative logic prove that positive 'OR' is equal to negative 'AND'. (05 Marks)
c. What are Hazards? Briefly describe about designing Hazard free circuit. (05 Marks)

OR

- 4 a. Give Sum-Of-Product (SOP) and Product-Of-Sum (POS) circuit for $f(A, B, C, D) = \sum m(6, 8, 9, 10, 11, 12, 13, 14, 15)$. (06 Marks)
b. Explain the verilog program structure. (05 Marks)
c. Design a logic circuit to provide an output when any two or three of four switches are closed. (05 Marks)

Module-3

- 5 a. Implement the following Boolean function using 4:1 multiplexer $F(A, B, C, D) = \sum m(0, 1, 2, 4, 6, 9, 12, 14)$. (06 Marks)
b. Construct 16:1 multiplexer using 4:1 and 2:1 multiplexer. (05 Marks)
c. What is a decoder? Give the circuit for 3:8 decoder. (05 Marks)

OR

- 6 a. What is a magnitude comparator? Explain a 1-bit comparator with truth table and circuit diagram. (06 Marks)
b. Briefly explain about parity generators and checkers. For a 3 bit message, give the expression for even parity bit. (05 Marks)
c. Compare and contrast PLA and PAL. (05 Marks)

Module-4

- 7 a. Explain the working of JK master slave flip-flop with a sketch, truth table and symbol. (06 Marks)
b. Give a brief account an flip flop as finite state machine. (05 Marks)
c. Briefly describe about sequential logic circuit. (05 Marks)

OR

- 8 a. Enumerate different types of shift registers. Explain Serial In Serial Out (SISO) register. (06 Marks)
b. Mention the applicators of shift registers. (05 Marks)
c. Using behavioral model write verilog HDL code for a 'D' flipflop with reset input. (05 Marks)

Module-5

- 9 a. Explain digital clock with block diagram. (06 Marks)
b. Design a 3 bit synchronous binary counter using JK flip flop. (05 Marks)
c. Mention different types of A/D converters and test its specifications. (05 Marks)

OR

- 10 a. Explain binary weighted resistor D/A converter. Mention its drawbacks. (06 Marks)
b. Describe about successive approximation type ADC. (05 Marks)
c. What is the resolution of a 12 bit D/A converter which uses a binary ladder, if the full scale output is +10V? (05 Marks)

* * * * *